

Experiment No:

Date:


Potentiometer I

Aim:

To compare the emf's of two primary cells using Potentiometer

Apparatus:

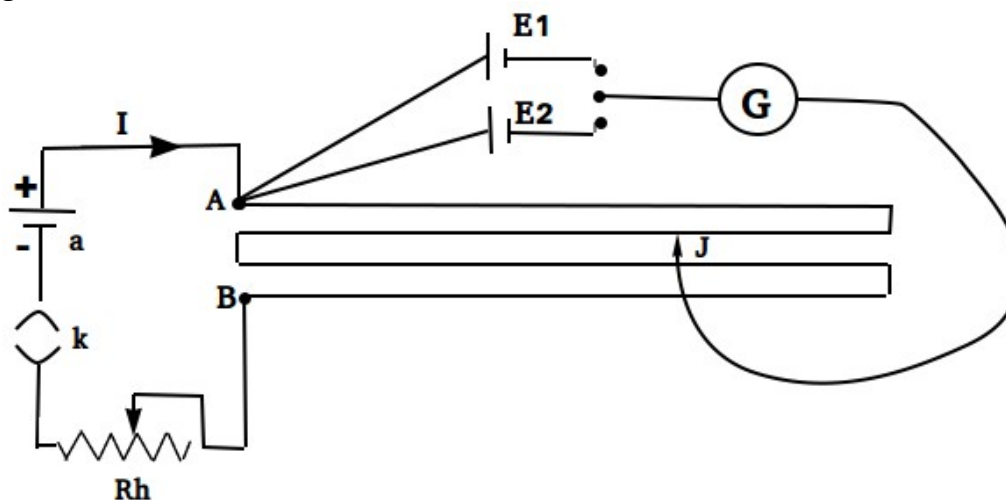Potentiometer, Accumulator, Daniel Cell, Leclanche Cell, Rheostat, Key, Jockey, Connecting wires etc.



Theory:

When a steady current flows through a resistance wire, the potential difference developed in the wire is directly proportional to the length of the wire,

If E_1 and E_2 are the emf's of a Daniel Cell and Leclanche Cell and l_1 and l_2 are their respective balancing lengths, then

$$E_1 \propto l_1 \text{ and } E_2 \propto l_2$$

that is
$$\frac{E_1}{E_2} = \frac{l_1}{l_2}$$

Observations:

Sl No	Balancing Length for (cm)		$\frac{E_1}{E_2} = \frac{l_1}{l_2}$
	Daniel Cell (E_1)	Leclanche Cell	
1			
2			
3			
4			
5			
6			
7			

The Ratio of emf's =

Result:

The Ratio of emf's =